

Question 1

[20 marks]

Calculate the fan-out of the DTL gate shown in Fig. 1, assuming $V_{CC} = 5\text{ V}$, $R_1 = 2\text{ k}\Omega$, $R_2 = 2\text{ k}\Omega$, $R_3 = 1\text{ k}\Omega$, $R_4 = 1\text{ k}\Omega$, $V_{D(ON)} = V_{BE(sat)} = 0.7\text{ V}$, $V_{CE(sat)} = 0.2\text{ V}$, $\beta_F = 20$, and $\beta_R = 0.2$.


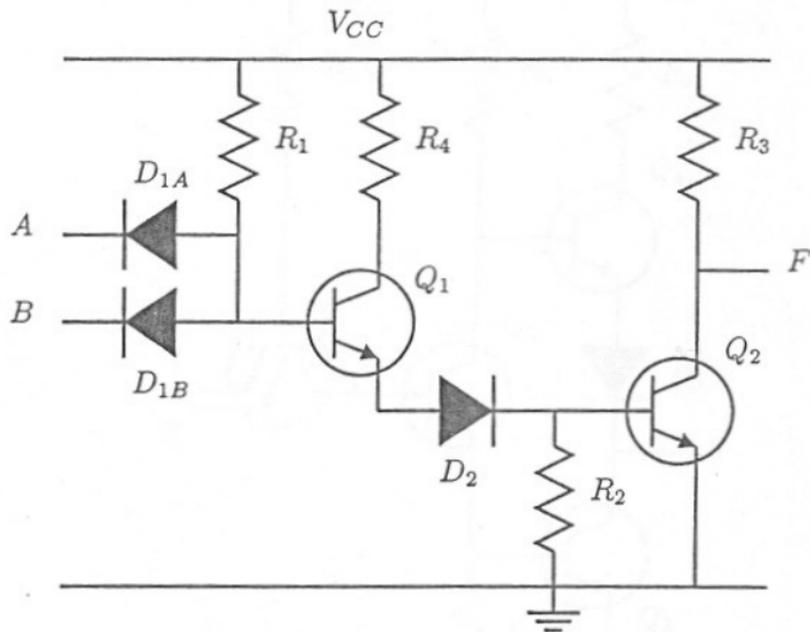


Figure 1

DTL gate fan-out.

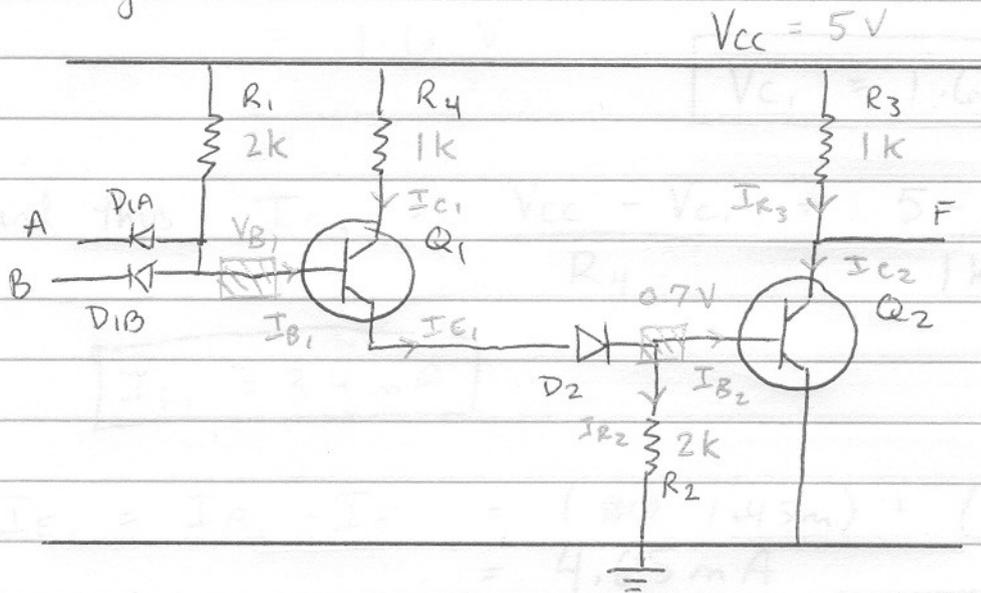

$$V_{D(on)} = V_{BE(sat)} = 0.7 \text{ V}$$

$$V_{CE(sat)} = 0.2 \text{ V}$$

$$\beta_F = 20$$

$$V_{B1} = V_{BE(sat)_2} + V_{D2} + V_{BE(sat)_1}$$

$$= 3(0.7) = 2.1 \text{ V}$$

$$V_{B1} = 2.1 \text{ V}$$

$$I_{B1} = \frac{V_{CC} - V_{B1}}{R_1} = \frac{5 - 2.1}{2k} = 1.45 \text{ mA}$$

$$I_{B1} = 1.45 \text{ mA}$$

Now, assuming Q1 not saturated

$$I_{C1} = \beta_F I_{B1} = (20)(1.45 \text{ mA}) = 29 \text{ mA}$$

$$I_{C1} = 29 \text{ mA}$$

Check:

$$V_{B1} = V_{CC} - R_4 I_{C1} = 5 - (1k)(29 \text{ mA})$$

$$= -24 \text{ V}$$

Therefore

Q1 IS saturated

$$\begin{aligned} \text{So, } V_{C_1} &= V_{BE(\text{sat})_2} + V_D + V_{CE(\text{sat})_1} \\ &= 0.7 + 0.7 + 0.2 \\ &= 1.6 \text{ V} \end{aligned}$$

$$V_{C_1} = 1.6 \text{ V}$$

$$\text{and thus } I_{C_1} = \frac{V_{CC} - V_{C_1}}{R_4} = \frac{5 - 1.6}{1\text{k}} = 3.4 \text{ mA}$$

$$I_{C_1} = 3.4 \text{ mA}$$

$$\begin{aligned} I_{E_1} &= I_{B_1} + I_{C_1} = (\text{~~2.4~~ } 1.45\text{m}) + (3.4\text{m}) \\ &= 4.85 \text{ mA} \end{aligned}$$

$$I_{E_1} = 4.85 \text{ mA}$$

$$I_{B_2} = I_{E_1} - I_{R_2}$$

$$I_{R_2} = \frac{V_{BE(\text{sat})_2} - 0}{R_2} = \frac{0.7}{2\text{k}} = 0.35 \text{ mA}$$

$$I_{B_2} = 4.85\text{m} - 0.35\text{m} = 4.5 \text{ mA}$$

$$I_{B_2} = 4.5 \text{ mA}$$

$$\begin{aligned} I_{C_2(\text{max})} &= \beta_F I_{B_2} = (20)(4.5\text{m}) \\ &= 90 \text{ mA} \end{aligned}$$

$$I_{C_2(\text{max})} = 90 \text{ mA}$$

$$I_{R_3} = \frac{V_{CC} - V_{CE(\text{sat})_2}}{R_3} = \frac{5 - 0.2}{1} = 4.8 \text{ mA}$$

$$I_{R_3} = 4.8 \text{ mA}$$

$$I_{\text{LOAD}} = \frac{V_{CC} - V_{CE(\text{sat})_2} - V_D}{R_1} = \frac{5 - 0.9}{2\text{k}} = 2.05 \text{ mA}$$

$$I_{\text{LOAD}} = 2.05 \text{ mA}$$

SPR Q1

$$I_{C2(\max)} = N \cdot I_{LOAD} + I_{R3}$$

$$90 \text{ mA} = N \cdot (2.05 \text{ mA}) + (4.8 \text{ mA})$$

$$N = \frac{90 \text{ mA} - 4.8 \text{ mA}}{2.05 \text{ mA}} = 41.56$$

$$N = 41$$

Q completed in 14:48

$$V_B = V_{BE} = V_{BE} + V_{BE(\text{sat})}$$
$$= 3(0.7) = 2.1 \text{ V}$$

$$V_B = 2.1 \text{ V}$$

$$I_B = \frac{V_{CC} - V_B}{R_B} = \frac{5 - 2.1}{2 \text{ k}\Omega} = 1.45 \text{ mA}$$

$$I_B = 1.45 \text{ mA}$$

Now, assuming Q, not saturated

$$I_{C1} = \beta_F I_B = (20)(1.45 \text{ mA}) = 29 \text{ mA}$$

$$I_{C1} = 29 \text{ mA}$$

Check:

$$V_B = V_{CC} - R_B I_{C1} = 5 - (1 \text{ k}\Omega)(29 \text{ mA})$$
$$= -24 \text{ V}$$

Therefore

Q, IS Saturated