
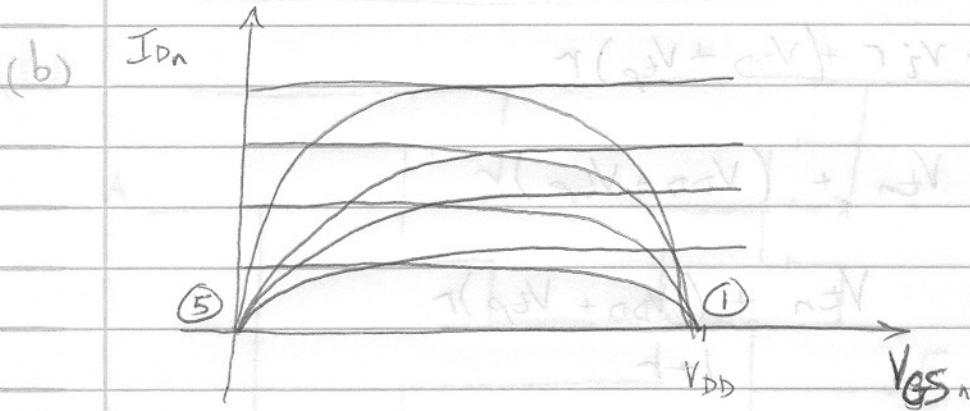



Not gate

EXAM READY ANSWER

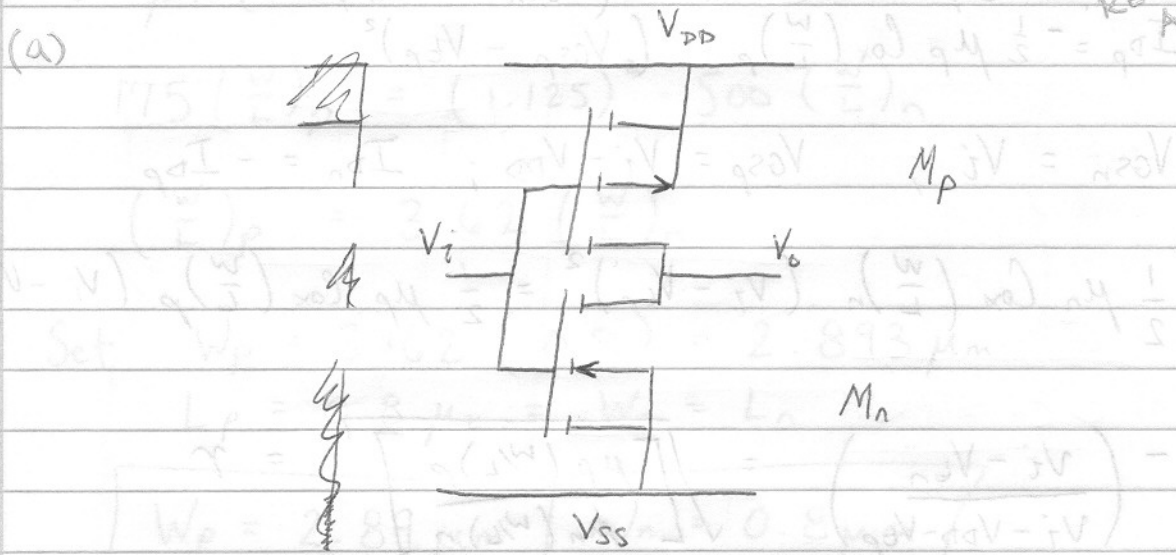

The operating point is given by the intersection of the curves

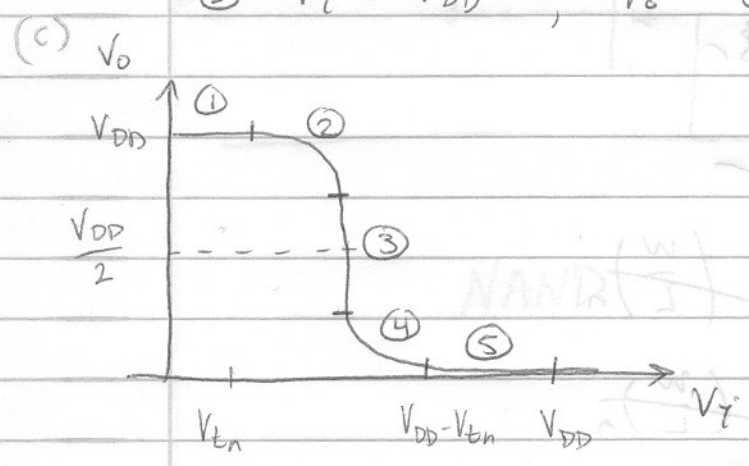- ①  $V_i = 0$  ,  $V_o = V_{DD}$
- ⑤  $V_i = V_{DD}$  ,  $V_o = 0$



- ①  $M_n$  cutoff,  $M_p$  triode
- ②  $M_n$  saturated,  $M_p$  triode
- ③  $M_n$  saturated,  $M_p$  saturated
- ④  $M_n$  triode,  $M_p$  saturated
- ⑤  $M_n$  triode,  $M_p$  cutoff

$$(d) \quad I_{Dn} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_n (V_{GSn} - V_{tn})^2$$

$$I_{Dp} = -\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_p (V_{GSp} - V_{tp})^2$$

$$V_{GSn} = V_i; \quad V_{GSp} = V_i - V_{DD}; \quad I_{Dn} = -I_{Dp}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_n (V_i - V_{tn})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_p (V_i - V_{DD} - V_{tp})^2$$

$$-\left(\frac{V_i - V_{tn}}{V_i - V_{DD} - V_{tp}}\right) = \sqrt{\left[\frac{\mu_p (W/L)_p}{\mu_n (W/L)_n}\right]} = r$$

$$V_i - V_{tn} = -V_i r + (V_{DD} + V_{tp}) r$$

$$V_i (1+r) = V_{tn} + (V_{DD} + V_{tp}) r$$

$$V_i = V_{th} = \frac{V_{tn} + (V_{DD} + V_{tp}) r}{1+r}$$

$$(e) \quad V_{th} = \frac{V_{DD}}{2} = 2.5 = \frac{0.7 + (5 + (-0.9)) r}{1+r}$$

$$2.5 (1+r) = 0.7 + 4.8 r$$

$$2.5 + 2.5r = 0.7 + 4.8 r$$

$$1.8 = 1.6 r$$

$$\boxed{r = 1.125}, \quad \text{Then}$$

$$\mu_p \left(\frac{W}{L}\right)_p = \mu_n \left(\frac{W}{L}\right)_n$$

$$175 \left(\frac{W}{L}\right)_p = 500 \left(\frac{W}{L}\right)_n$$

$$\left(\frac{W}{L}\right)_p = 2.86 \left(\frac{W}{L}\right)_n$$

$$\sqrt{\frac{\mu_p (W/L)_p}{\mu_n (W/L)_n}} = 1.125$$

$$175 \left(\frac{W}{L}\right)_p = (1.125)^2 \cdot 500 \left(\frac{W}{L}\right)_n$$


$$\left(\frac{W}{L}\right)_p = 3.62 \left(\frac{W}{L}\right)_n$$

Set  $W_p = 3.62 (0.8) = 2.893 \mu\text{m}$

$$L_p = 0.8 \mu\text{m} = W_n = L_n$$

$W_p = 2.89 \mu\text{m}$	$W_n = 0.8 \mu\text{m}$
--------------------------	-------------------------

(f)

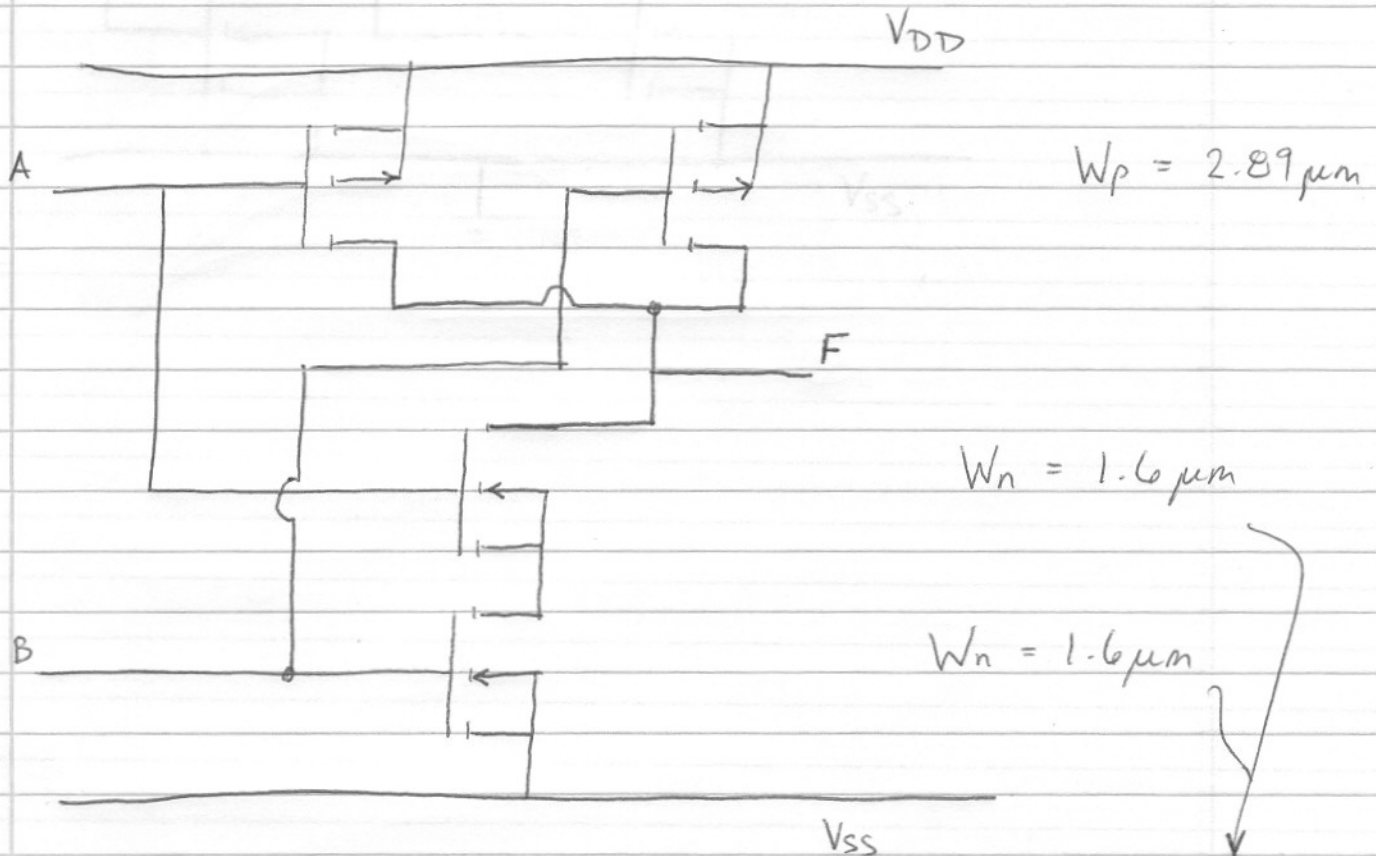


NAND

compensates for effectively being twice as long!

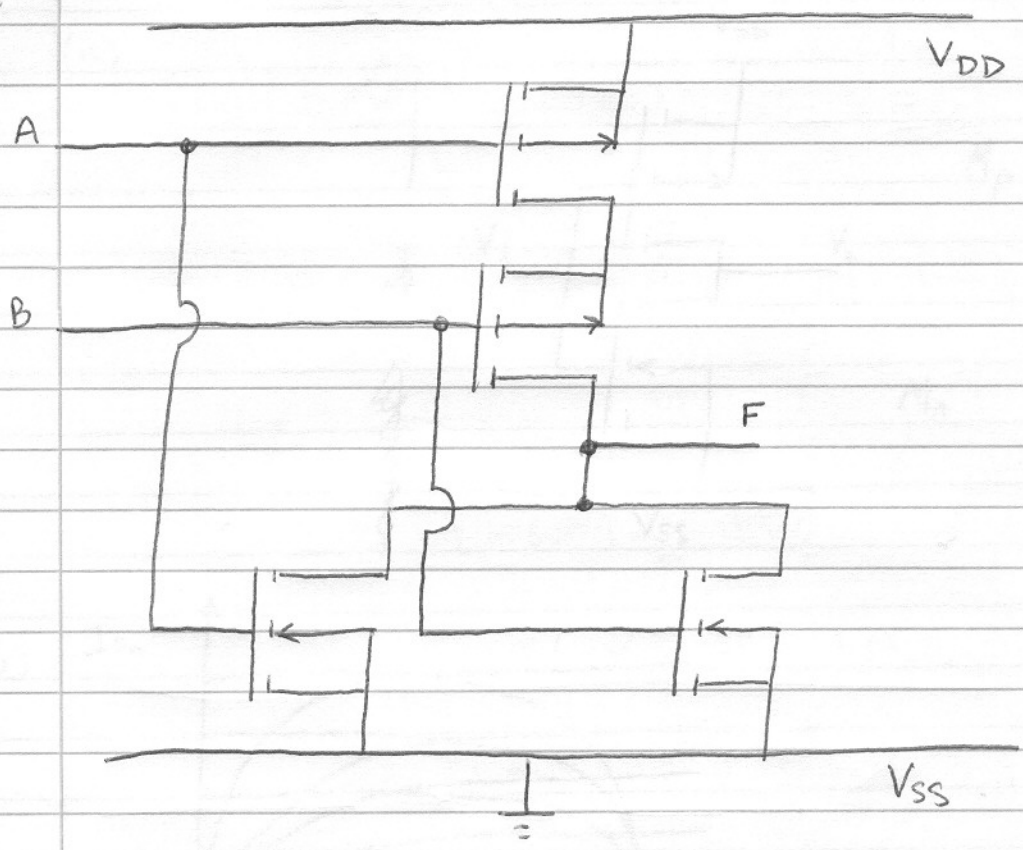(f)  
ALT.


Alternatively, may be asked for a NOR gate



twice as long  
~~wide~~ effectively  
→ need  $2W_p$   
for ea. of these  
to maintain  
 $V_{th} = V_{DD}/2$

The operating point is given by the intersection of the curves

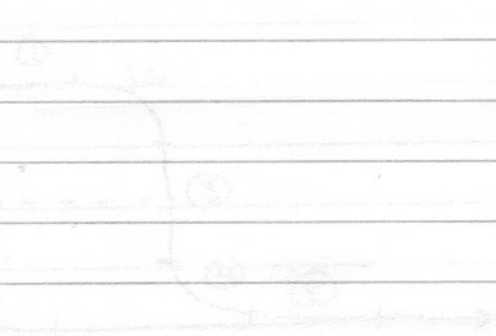- ①  $V_1 = 0$        $V_2 = V_{DD}$
- ②  $V_1 = V_{DD}$      $V_2 = 0$



- ③  $M_n$  cutoff,  $M_p$  triode
- ④  $M_n$  saturated,  $M_p$  triode
- ⑤  $M_n$  saturated,  $M_p$  saturated
- ⑥  $M_n$  triode,  $M_p$  saturated
- ⑦  $M_n$  triode,  $M_p$  cutoff