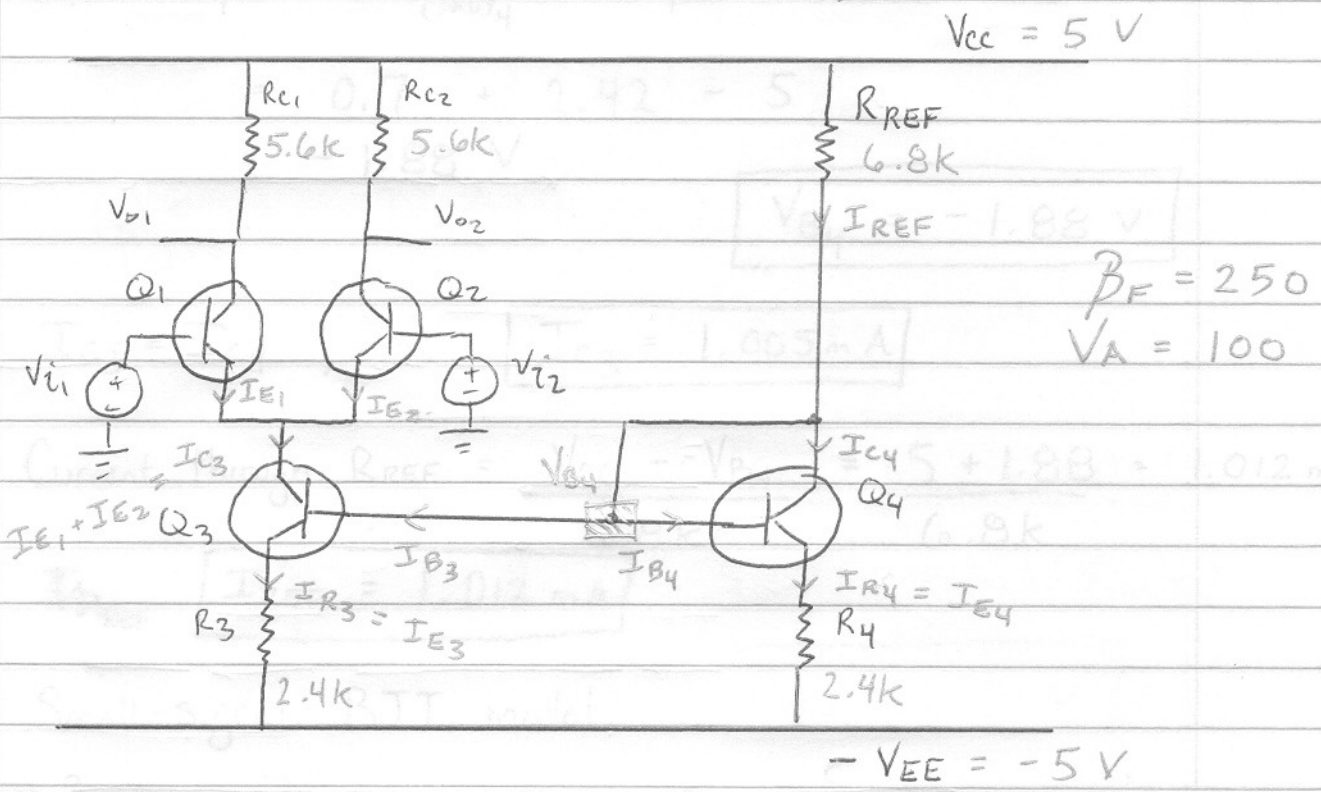


ALMOST EXAM WORTHY
→ NEED TO CHECK



(a)

$$I_{REF} = I_{C4} + I_{B4} + I_{B3} \quad \text{but} \quad I_{C4} = \beta_F I_{B4}$$

$$= (1 + \beta_F) I_{B4} + I_{B3}$$

$$= (2 + \beta_F) I_{B4}$$

$$I_{REF} = 252 I_{B4}$$

$$10 - 0.7 = (2 + \beta) I_{B4} R_{REF} + (1 + \beta) I_{B4} R_4$$

$$9.3 = (252) I_{B4} (6.8k) + (251) I_{B4} (2.4k)$$

$$9.3 = (1713.6k) I_{B4} + (602.4k) I_{B4}$$

$$\frac{9.3}{2316k} = I_{B4}$$

$$I_{B4} = 4.02 \mu A$$

$$I_{C4} = \beta_F I_{B4} = (250)(4.02 \mu A)$$

$$= 1.005 \text{ mA}$$

$$I_{C4} = 1.005 \text{ mA}$$

$$I_{E4} = I_{B4} + I_{C4} = 1.00902 \text{ mA}$$

$$I_{E4} = 1 \text{ mA}$$

$$V_{R4} = I_{R4} \cdot R_4 = 2.42 \text{ V} \quad \text{dropped across } R_4$$

$$\text{So, } V_{B4} = V_{BE(sat)4} + V_{R4} - V_{EE} = \beta_F I_B$$

$$= 0.7 + 2.42 - 5$$

$$= -1.88 \text{ V}$$


$$V_{B4} = -1.88 \text{ V}$$

$$I_{C3} = I_{C4}, \text{ so } I_{C3} = 1.005 \text{ mA}$$

$$\text{Current through } R_{REF} = \frac{V_{CC} - V_{B4}}{6.8 \text{ k}} = \frac{5 + 1.88}{6.8 \text{ k}} = 1.012 \text{ mA}$$

$$I_{REF} = 1.012 \text{ mA}$$


Small-signal BJT model

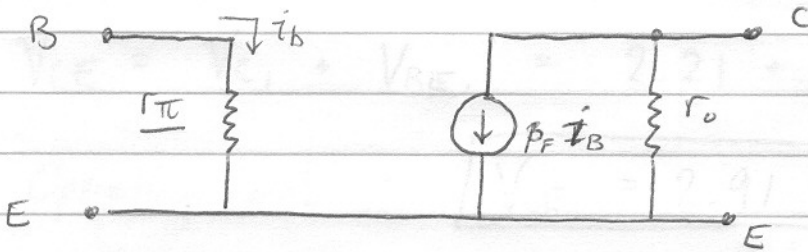

$$r_o = \frac{V_A}{I_C} = \frac{100}{1.012 \text{ mA}} = 98.8 \text{ k}\Omega$$

$$r_o = 98.8 \text{ k}\Omega$$

The equivalent circuit is:

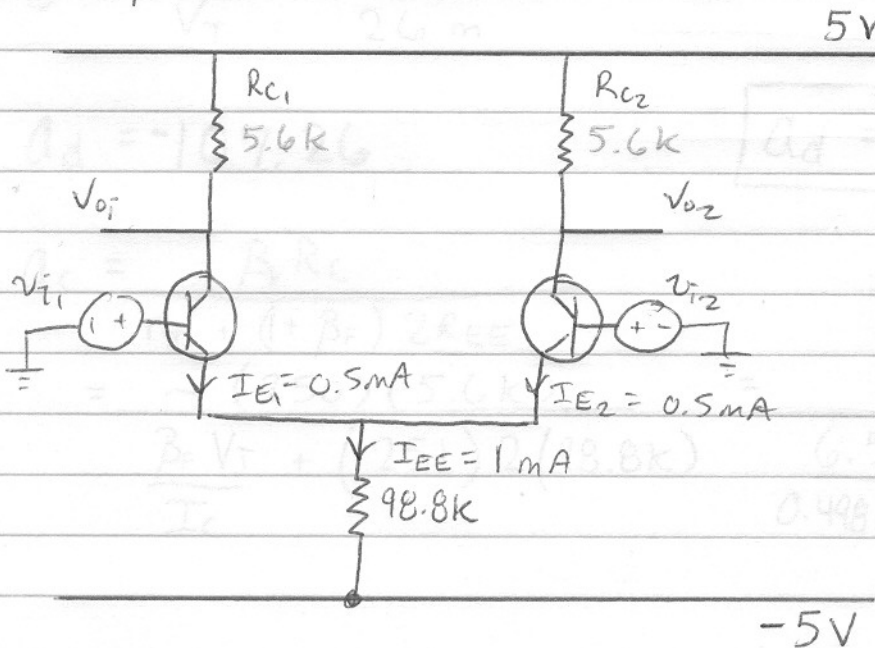

$$I_{E1} = I_{B1} + I_{C1}$$

$$I_{E1} = I_{C1} \left(1 + \frac{1}{\beta_F} \right)$$

$$(0.5 \text{ mA}) = I_{C1} \left(1 + \frac{1}{250} \right)$$

$$I_{C1} = \frac{0.5 \text{ mA}}{1.004} = 4.98 \times 10^{-4} = 0.498 \text{ mA}$$

$$I_{C1} = 0.498 \text{ mA}$$

$$V_{C1} = V_{CC} - I_{C1} R_{C1} = 5 - (0.498 \text{ mA})(5.6 \text{ k})$$
$$= 2.21 \text{ V}$$

$$V_{C1} = 2.21 \text{ V}$$

$$V_{CE} = V_{C1} + V_{BE1} = 2.21 + 0.7 = 2.91 \text{ V}$$

$$\text{Operating Point} = V_{CE1} = 2.91 \text{ V} *$$

$$(b) \quad a_d = \frac{-\beta_F R_c}{r_{\pi}} = -g_m R_c = -0.02 R_c$$
$$= -0.02 (5.6 \text{ k})$$
$$= -107.26$$

$$g_m = \frac{I_c}{V_T} = \frac{0.498 \text{ mA}}{26 \text{ mV}} = 0.02$$

$$a_d = -107.26$$

$$a_d = -107.26$$

$$(c) \quad a_c = \frac{-\beta_F R_c}{r_{\pi} + (1 + \beta_F) 2R_{EE}}$$
$$= \frac{-(250)(5.6 \text{ k})}{\frac{\beta_F V_T}{I_c} + (251) 2(98.8 \text{ k})} = \frac{-1400 \text{ k}}{6.5 + (251)(197.6 \text{ k})}$$
$$= \frac{-1400 \text{ k}}{0.498 \text{ mA}}$$

$$= \frac{-1400 \text{ k}}{13052.2 + 49597.6 \text{ k}} = \frac{-1400 \text{ k}}{13.0522 \text{ k} + 49597.6 \text{ k}}$$

$$= \frac{-1400}{49610.65} = -0.0282$$

$$a_c = -0.0282$$

$$(d) \text{ CMRR} = \frac{|a_d|}{|a_c|} = \frac{|-107.26|}{|-0.0282|} = 3803.55$$

$$\text{CMRR (in dB)} = 20 \log(3803.55)$$

$$= 71.6 \text{ dB}$$

$$\text{CMRR} = 3803.6$$

$$\text{in dB} = 71.6 \text{ dB}$$

$$\text{CMRR (in dB)} = 71.6 \text{ dB}$$

$$10 - 0.7 = (2 + \beta) I_{B4} R_{EE} + (\beta) I_{B4} R_4$$

$$9.3 = (254) I_{B4} (6.5 \text{ k}) + (251) I_{B4} (2.4 \text{ k})$$

$$9.3 = (1713.6 \text{ k}) I_{B4} + (602.4 \text{ k}) I_{B4}$$

$$9.3 = I_{B4}$$

$$2316 \text{ k}$$

$$I_{B4} = 4.02 \mu\text{A}$$

$$I_{E4} = \beta I_{B4} = (250)(4.02 \mu\text{A}) = 1.005 \text{ mA}$$

$$I_{E4} = 1.005 \text{ mA}$$

$$I_{E4} = I_{B4} + I_{E4} = 1.00902 \text{ mA}$$

$$I_{E4} = 1 \text{ mA}$$

$$V_{E4} = I_{E4} \cdot R_4 = 2.42 \text{ V dropped across } R_4$$