

**OLLSCOIL NA hEIREANN, CORCAIGH
THE NATIONAL UNIVERSITY OF IRELAND, CORK**

**COLAISTE NA hOLLSCOILE, CORCAIGH
UNIVERSITY COLLEGE, CORK**

SUMMER 2002

B.E. DEGREE (ELECTRICAL)

APPLIED POWER ELECTRONICS AND MOTION CONTROL (EE4001)

Prof. G. Irwin
Prof. R. Yacamini
Dr. J.G. Hayes

Time Allowed – 3 Hours

Attempt **all five** questions. Each question carries equal marks.

The use of non-programmable electronic calculators is permitted.

Question 1 - DC Motor and Power Electronics

The system parameters of a permanent-magnet dc motor supplied by a switch-mode PWM dc-dc converter are as follows: armature resistance $R_a = 0.35 \Omega$, armature inductance $L_a = 1.5$ mH, motor moment of inertia 0.02 kg m^2 , motor voltage constant $k_E = 0.5 \text{ V/(rad/s)}$, converter dc bus voltage $V_d = 200 \text{ V}$, switching frequency $f_s = 25 \text{ kHz}$, and amplitude of triangular waveform control voltage $V_{tri} = 3 \text{ V}$. The motor is spinning in a forward direction at a speed of 1500 RPM and supplies a load torque of 10 Nm.

- A. Calculate the following: (i) the applied armature voltage V_{AB} ; (ii) duty ratios for (a) overall converter, (b) pole A, and (c) pole B; and (iii) the peak-to-peak ripple on the armature current.
- B. Sketch the waveforms for the triangular voltage $v_{tri}(t)$, control voltage $v_c(t)$, pole A voltage $v_A(t)$, the pole B voltage $v_B(t)$, armature voltage $v_{AB}(t)$, armature current $i_a(t)$ and the dc bus current $i_d(t)$.

Question 2 – Mechanical Systems and PMAC Motor

- A. An electric vehicle has the following attributes: mass $M = 1400$ kg, drag co-efficient $C_W = 0.19$, vehicle cross section $A = 2.4$ m², co-efficient of rolling resistance $C_{RR} = 0.0044$, wheel diameter $d_w = 0.6$ m, gear ratio from rotor to drive axle $n = 10.946$, and a nominal gear efficiency of 95%. Neglect internal moment of inertia and use density of air $\rho_{\text{air}} = 1.202$ kg m⁻³.
The vehicle is required to accelerate from 0 to 100 km/hr in 8 s on a flat road surface under calm wind conditions. Instantaneously at 60 km/hr, calculate (i) the aerodynamic drag, (ii) the rolling resistance, (iii) the acceleration force, and (iv) the electromagnetic torque required from the rotor.
- B. A four-pole three-phase permanent-magnet ac motor is used for traction in a hybrid-electric vehicle. The vector-controlled motor is rated at 100 Nm at 6000 rpm, and is powered by a three-phase sinusoidal PWM inverter supplied by a 300 V NiMH battery pack. The motor efficiency and power factor at rated power are 90% and 0.9, respectively. Determine the following drive parameters at rated power and speed:
- per-phase voltage, V_{ph} ,
 - per-phase back emf, E_{ph} ,
 - per-phase current, I_{ph} ,
 - per-phase synchronous inductance, L_S ,
 - motor voltage and torque constants, k_E and k_T ,
 - motor copper loss, given a per-phase series resistance of $R_S = 15$ m Ω ,
 - core, friction and windage losses for the machine.

Question 3 – Power Semiconductors

The IRFP460 power MOSFET from International Rectifier operates in a boost converter switching at 20 kHz with a dc link voltage $V_d = 400$ V, and load current $I_o = 20$ A. The MOSFET is driven by a voltage-source square wave v_{GG} , of amplitude 0 V to 15 V, in series with an external gate resistance $R_G = 25$ Ω . Assume the boost diode has a 1V forward drop and no reverse recovery.

- Sketch $v_{GG}(t)$, $v_{GS}(t)$, $v_{DS}(t)$, and $i_D(t)$ during turn-on of the MOSFET.
- Determine the following parameters from the data sheet at a junction temperature of 80°C: threshold voltage, forward transconductance, gate-source capacitance, gate-drain capacitance, and on-state resistance.
- Calculate the following (i) turn-on delay time t_{don} , (ii) current rise time t_{ir} , (iii) voltage fall time t_{fv} and (iv) turn-on energy loss.

Question 4 – Induction Motor

A symmetrical, four-pole, three-phase, wye-connected induction motor is characterized as follows. The dc phase-to-phase resistance is measured to be 1.1Ω . A no-load test with an applied voltage of 208 V (line-line), 60 Hz, results in a phase current of 6.5 A, and a three-phase power of 175 W. A locked-rotor test with an applied voltage of 53 V (line-line), 60 Hz, results in a phase current of 18.2 A, and a three-phase power of 900 W.

- Estimate the per-phase equivalent circuit parameters: R_S , L_{LS} , L_M , L_{LR}' , and R_R' .
- When supplied by a current-controlled inverter operating at 60 Hz, the motor generates a torque of 50 Nm at 1764 rpm. Estimate (i) the sum of the core and mechanical power losses, and (ii) the per-phase rotor current.
- Determine approximate values for the applied per-phase voltage, per-phase current and power factor.

Question 5 – Controller Design

The system parameters of a permanent-magnet dc motor supplied by a switch-mode PWM dc-dc converter are as follows: armature resistance $R_a = 2 \Omega$, electrical time constant $\tau_e = 0.5$ ms, motor voltage constant $k_E = 0.2$ V/(rad/s), controller IC UC3637, armature current transducer LA 03-PB, input control ± 2 V to output an torque of ± 0.4 Nm. Torque is controlled by regulating the armature current with a proportional-integral controller. The feedback effects of the motor-induced back emf and the load torque on the control loop can be neglected.

- Referring to the schematic in Fig. 1 determine (i) the amplitude of triangular waveform control voltage, V_{TH} , (ii) switching frequency, f_s , (iii) the gain of the PWM power amplifier, and (iv) the gain of the feedback stage.
- Sketch a block diagram of the current-control loop.
- Derive the open-loop gain function of the current loop.
- Calculate the values of the error amplifier compensation components R_I , R_F , and C_F selecting the current loop crossover frequency to be one tenth of the switching frequency, and the phase margin to be 45° .

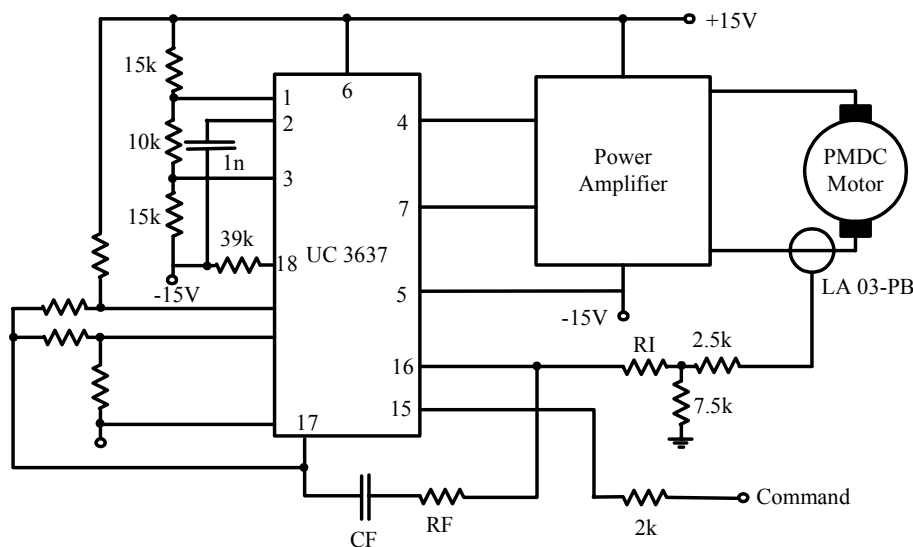


Figure 1